

1	B is the correct answer as it is a $V-I$ graph for a filament lamp A is not the correct answer as it is not a $V-I$ graph for a diode C is not the correct answer as it is not a $V-I$ graph for an ohmic conductor D is not the correct answer as it is not a $V-I$ graph for a thermistor	(1)
---	--	-----

9	The only correct answer is A B is not correct because $W = VIt$ and area under graph = It C is not correct because $W = VIt$ and area under graph = It D is not correct because $W = VIt$ and area under graph = It	1
---	--	---

4	The only correct answer is A <i>B is not correct as it uses an incorrect expression.</i> <i>C is not correct as it uses an incorrect expression.</i> <i>D is not correct as it uses an incorrect expression.</i>	(1)
---	---	-----

5	A is the correct answer as $R = V/I$, and V is measured in JC^{-1} and I is measured in Cs^{-1}. B is not the correct answer as the units of resistance are not JC^2s^{-1} C is not the correct answer as the units of resistance are not $JC^{-1}s^{-1}$ D is not the correct answer as the units of resistance are not JCs	(1)
---	---	-----

19(a)	A <u>photon</u> (incident on a surface) is <u>absorbed</u> by an atom / electron (1) Or A <u>photon</u> (incident on a surface) collides with an atom / electron An electron gains energy and is emitted (from the surface) (1)	2
-------	---	---

19(b)	(To cause the photoelectric effect) the energy (of a photon) must be greater than the work function (of the photocathode) (1) Or (to cause the photoelectric effect) the frequency (of a photon) must be greater than the threshold frequency (of the photocathode) Photon energy is proportional to frequency, so photons below a certain frequency / energy cannot cause the photoelectric effect (1)	2
-------	--	---

19(c)	Use of $1 \text{ eV} = 1.6 \times 10^{-19} \text{ J}$ (1) Use of $E = hf$ (1) Use of $v = f\lambda$ (1) Comparison of 840 nm with 700 nm and conclusion all wavelengths of visible light can be detected (1) Or Comparison of $2.85 \times 10^{-19} \text{ J}$ with $2.37 \times 10^{-19} \text{ J}$ and conclusion all wavelengths of visible light can be detected Or Comparison of 1.78 eV with 1.48 eV and conclusion all wavelengths of visible light can be detected Or Comparison of $3.57 \times 10^{14} \text{ Hz}$ with $4.29 \times 10^{14} \text{ Hz}$ <u>Example calculation</u> $E = 1.48 \text{ eV} \times 1.6 \times 10^{-19} \text{ J eV}^{-1} = 2.37 \times 10^{-19} \text{ J}$ $f_{\text{threshold}} = \frac{2.37 \times 10^{-19} \text{ J}}{6.63 \times 10^{-34} \text{ Js}} = 3.57 \times 10^{14} \text{ Hz}$ $\lambda_{\text{threshold}} = \frac{3 \times 10^8 \text{ m s}^{-1}}{3.57 \times 10^{14} \text{ Hz}} = 840 \times 10^{-9} \text{ m}$ 700 nm < 840 nm so all wavelengths of visible light can be detected	4
-------	--	---

19(d)	Use of $E_k = \frac{1}{2} mv^2$ (1) Use of $V = \frac{W}{Q}$ (1) Final kinetic energy = $1.81 \times 10^{-17} \text{ (J)}$ (1) <u>Example calculation</u> Initial $E_k = 0.5 \times 9.11 \times 10^{-31} \text{ kg} \times (1.35 \times 10^6 \text{ m s}^{-1})^2 = 8.30 \times 10^{-19} \text{ J}$ $W = 108 \text{ V} \times 1.6 \times 10^{-19} \text{ C} = 1.73 \times 10^{-17} \text{ J}$ Final kinetic energy (= $1.73 \times 10^{-17} \text{ J} + 8.30 \times 10^{-19} \text{ J}$) = $1.81 \times 10^{-17} \text{ J}$	3
-------	--	---

19(e)	EITHER	
	Use of $V = IR$ to calculate current in circuit	(1)
	Calculates total p.d across resistors A to D	(1)
	Use of sum of e.m.f. = sum of p.d	(1)
	Internal resistance = $1.20 \text{ M}\Omega$	(1)
	OR	
	Calculates total p.d. across resistors A to D	(1)
	Uses ratio of resistance = ratio of p.d.	(1)
	Correct values substituted into ratio equation	(1)
	Internal resistance = $1.20 \text{ M}\Omega$	(1)
	<u>Example calculation</u>	
	$I = \frac{108 \text{ V}}{85 \times 10^3 \Omega} = 1.27 \times 10^{-3} \text{ A}$	
	$V = 1960 - 4 \times 108 = 1530 \text{ V}$	
	$r = \frac{1530 \text{ V}}{1.27 \times 10^{-3} \text{ A}} = 1.20 \times 10^6 \Omega$	
		4

Question Number	Answer	Mark
14 (a)	Use of e.m.f. = sum of p.d.s (1) Use of $V = IR$ (1) $r = 17\,000 \text{ } (\Omega)$ (1) <u>Example of calculation</u> $1.79 \text{ V} = 1.72 \text{ V} + (4.20 \text{ } \mu\text{A} \times r)$ $r = 16\,700 \text{ } (\Omega)$	3
14 (b)	Use of $P = IV$ with $V=1.72 \text{ (V)}$ (1) $P = 7.2 \times 10^{-6} \text{ W}$ (1) <u>Example of calculation</u> $P = 4.20 \text{ } \mu\text{A} \times 1.72 \text{ V}$ $P = 7.2 \times 10^{-6} \text{ W}$	2
14 (c)	Resistance of voltmeter very large Or $R \gg r$ Or internal resistance much less than resistance of voltmeter (1) (So) I very small [accept $I = 0$] (1) (So) Ir very small Or lost volts ≈ 0 Or $Ir \ll \mathcal{E}$ (1) (So) V (approximately) equal to e.m.f. (1)	4
	Total for question 14	9

11 (a)	The p.d. (across component) can be (reduced to) zero	(1)	1
11 (b)	Use of $R = \rho l/A$ Use of $A = \pi r^2$ Diameter = $1.8 \times 10^{-4} \text{ m}$ <u>Example of calculation</u>	(1) (1) (1)	3

	$24 \Omega = 1.2 \times 10^{-6} \Omega \text{ m} \times 0.5 \text{ m} \div A$ $A = 2.5 \times 10^{-8} \text{ m}^2$ $r = \sqrt{(2.5 \times 10^{-8} \text{ m}^2 \div \pi)} = 8.9 \times 10^{-5} \text{ m}$ $d = 1.78 \times 10^{-4} \text{ m}$		
11 (c)	Use of ratio lengths:voltages Or Use of ratio lengths:resistances Or See $I = 0.24 \text{ (A)}$ p.d. = 2.1 V <u>Example of calculation</u> $V = 12.0 \text{ V} \times 7.16 \text{ cm} / 40.0 \text{ cm} = 2.15 \text{ V}$	(1) (1)	2
	Total for question 11		6